

CND 111: Digital IC Design

Assignment #: 4

Section #: 16

Submitted by:

Student Name	ID
Aya Ahmed Abdelrahman	V23010284
Karim Mahmoud Kamal	V23010174
Nada Abdelkader Sharaf	V23010519
Kholoud Rafat	V23010199

Submitted to TA: Mohamed Elshafey


Date: 12/10/2023

➤ Final Lab

```

M E:/AUC assignments/Digital/lab4/TB.v (/TOP_TB) - Default
Ln#
1 module TOP_TB ();
2   reg operand_A_TB;
3   reg operand_B_TB;
4   wire [6:0] Decimal_Num_TB;
5   TOP DUT ( operand_A_TB, operand_B_TB, Decimal_Num_TB );
6   reg [1:0] mem_in [3:0];
7   reg [6:0] mem_out [3:0];
8   task initialize;
9   begin
10    $readmemb("INPUT.txt",mem_in);
11    $readmemb("OUTPUT.txt",mem_out);
12  end
13 endtask
14 integer i;
15 initial
16 begin
17   initialize;
18   for (i = 0; i < 4 ; i = i + 1)
19   begin
20     {operand_A_TB,operand_B_TB} = mem_in [i]; #10;
21     if (Decimal_Num_TB == mem_out [i])
22       $display("Case %d Passed",i+1);
23     else
24       $display("Case %d Failed",i+1);
25   end
26   $stop;
27 end
28 endmodule

```

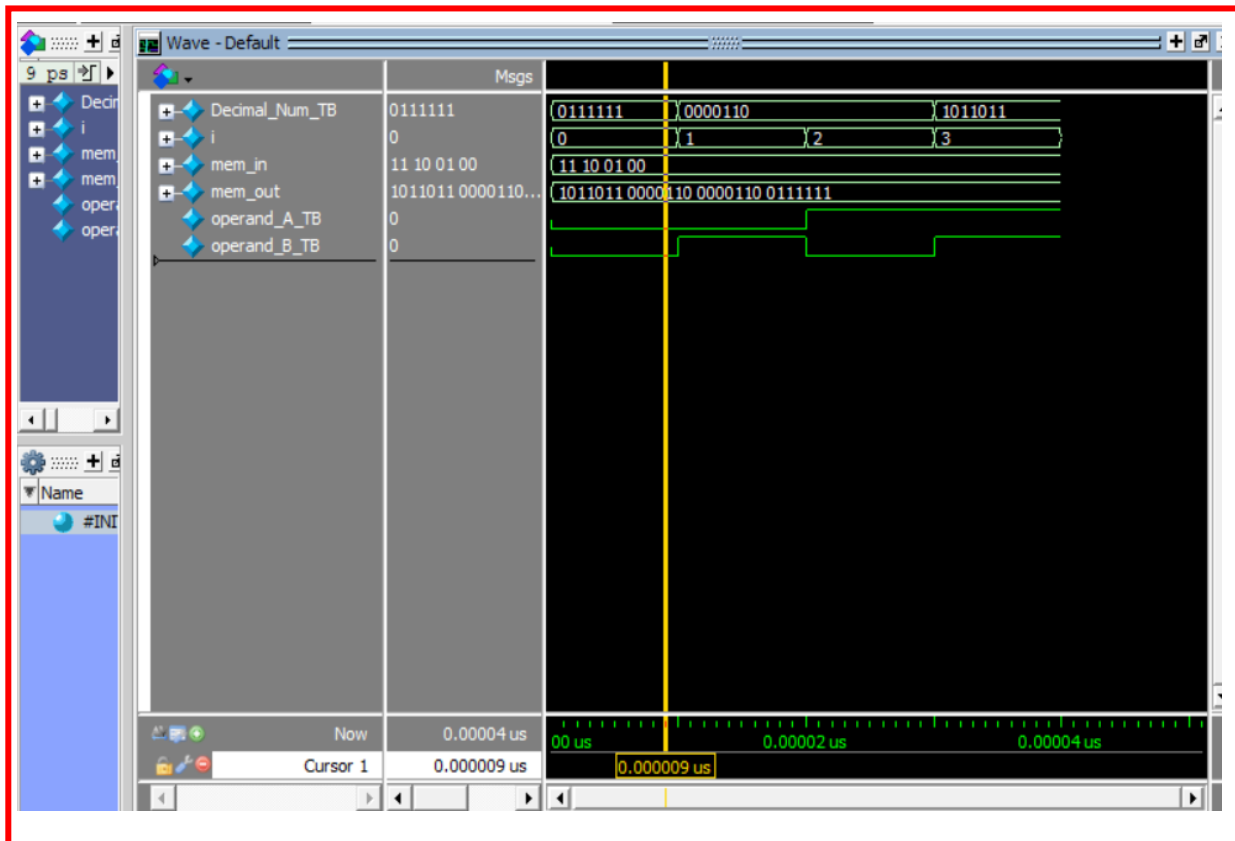


Comments

In this lab, the provided test bench is used to verify the functionality of the half adder and seven segments. The testbench reads input values from a file named "INPUT.txt" and expected output values from a file named "OUTPUT.txt" and compares them with the output produced by the DUT. The code defines a task named "initialize" that reads the contents of the "INPUT.txt" and "OUTPUT.txt" files into the mem_in and mem_out arrays, respectively. The code contains an initial block that executes the following steps:

- 1) Calls the initialize task to read input and output values from files.
- 2) Iterates a loop i from 0 to 3.
- 3) Assigns the values from mem_in to operand_A_TB and operand_B_TB.
- 4) Delays the simulation by 10-time units (#10).
- 5) Compares the value of Decimal_Num_TB with mem_out[i].
- 6) Displays a message indicating whether the test case passed or failed.

Assignment

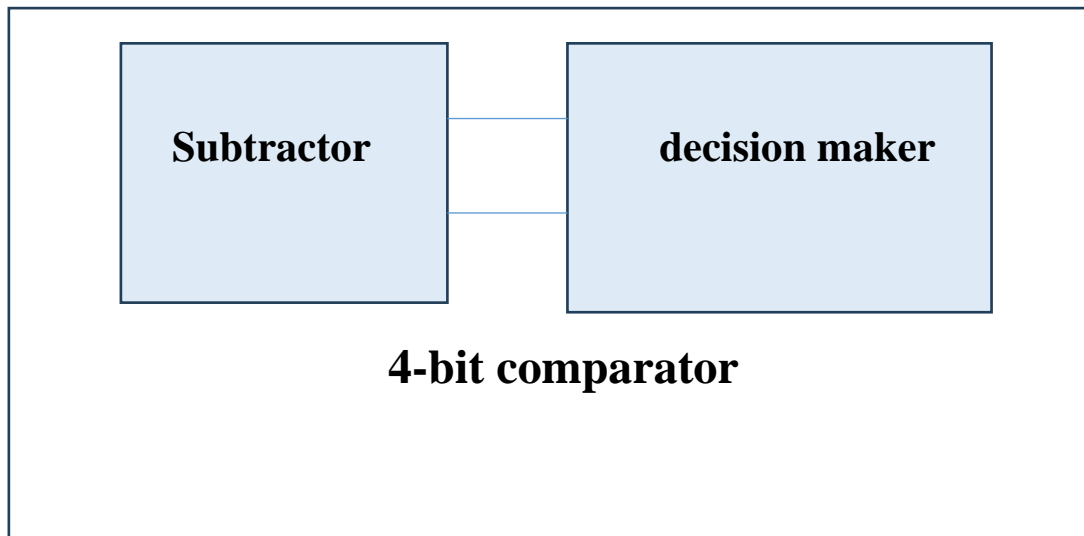

```
module half_adder ( a , b , sum , carry );  
  
    input a,b;  
    output sum, carry;  
  
    xor x1 ( sum, a , b );  
    and a1 ( carry , a , b );  
  
endmodule  
module full_adder ( in1 , in2 , Cin , sum , carry );  
  
    input in1, in2, Cin;  
    output sum, carry;  
    wire wsl, wcl, wc2;  
  
    half_adder hal ( in1 , in2 , wsl , wcl );  
    half_adder ha2 ( wsl , Cin , sum , wc2 );  
    or r1 ( carry , wcl , wc2 );  
  
endmodule  
module four_bit_comparator( x , y , v , n , z );  
  
    input [3:0] x;  
    input [3:0] y;  
    output v,n,z;  
    wire s0, s1, s2, s3;  
    wire c1, c2, c3, c4;  
  
    full_adder fa1 ( x[0] , ~y[0] , 1'b1 , s0 , c1 );  
    full_adder fa2 ( x[1] , ~y[1] , c1 , s1 , c2 );  
    full_adder fa3 ( x[2] , ~y[2] , c2 , s2 , c3 );  
    full_adder fa4 ( x[3] , ~y[3] , c3 , s3 , c4 );  
  
    nor nor1 ( z , s0 , s1 , s2 , s3 );  
    xor xor1 ( v , c3 , c4 );  
  
    assign n = s3;  
  
endmodule
```

Structural representation of 4-bit comparator.

```

M E:/AUC assignments/Digital/Comparator/Comparator.v - Default
Ln#
1 module four_bit_comparator_Cir1(input [3:0] A,B,
2   output Z,N,V);
3   assign Z=(A-B == 'b0) ? 1'b1: 1'b0;
4   assign V=(A>B) ? 1'b1:1'b0;
5   assign N=(A<B) ? 1'b1:1'b0;
6
7
8
9
10
11
12
13 endmodule


```

Behavioral representation of 4-bit comparator.

Comments

In the above two codes we tried to implement a 4-bit comparator using two methods (structural and behavioral). In the structural code representation, the modules work together to perform a four-bit comparison of the numbers x and y. The XOR gates compute the bitwise XOR of a and b, the AND gates compute the bitwise AND of a, b, and Cin, and the full adders perform the addition of the four-bit numbers, Then NOR gate checks the equality of x and y, and the XOR gate checks for overflow. The outputs v, n, and z provide information about the comparison result. In the behavioral representation, we compare the inputs A and B, if $A > B$ the output V will be equal to 1 else it will be equal to zero. For N, when the input $A < B$ it will be equal to 1 else it will be equal to zero. Finally, when the input $A = B$ the output Z will be equal to 1 else it will be equal to zero.

Structural View of 4bit Comparator

 

test bench

```
Ln#
1 module test_bench_comparator();
2
3     reg [3:0] x;
4     reg [3:0] y;
5     wire z,v,n;
6
7     integer counter;
8
9     four_bit_comparator four_bit_comparator1 ( x , y , v , n , z);
10
11 initial begin
12     counter=0;
13
14     /*-----First Test Case-----*/
15     #20;
16
17     x = 4'b0101;
18     y = 4'b0011;
19
20     #50;
21
22     $display( "inputA:%d , inputB:%d , z:%d , v:%d n:%d \n", $signed(x) , $signed(y) , $signed(z) , $signed(v) , $signed(n) );
23
24     if ( $signed(z) == 0 && $signed(n) == 0 && $signed(v) == 0 ) begin
25         $display( "TestCase# 1 : SUCCESS \n" );
26         counter=counter+1;
27     end
28     else begin
29         $display( "TestCase# 1 : FAILED \n" );
30     end
31
32     /*-----Second Test Case-----*/
33
34     #20;
35
36     x = 4'b0101;
37     y = 4'b0101;
38
39     #50;
```

```

40     $display( "inputA:%d , inputB:%d , z:%d , v:%d n:%d \n", x , y , z , v , n );
41
42     if ( z == 1 && n == 0 && v == 0 ) begin
43         $display( "TestCase# 2 : SUCCESS \n" );
44         counter=counter+1;
45     end
46     else begin
47         $display( "TestCase# 2 : FAILED \n" );
48     end
49
50     #100
51     $display( "The number of success test cases:%d \n", counter );
52
53     /*-----Second Test Case-----*/
54
55     #20;
56
57     x = 4'b0101;
58     y = 4'b0110;
59
60     #50;
61
62     $display( "inputA:%d , inputB:%d , z:%d , v:%d n:%d \n", x , y , z , v , n );
63
64     if ( z == 0 && n == 1 && v == 0 ) begin
65         $display( "TestCase# 3 : SUCCESS \n" );
66         counter=counter+1;
67     end
68     else begin
69         $display( "TestCase# 3 : FAILED \n" );
70     end
71
72     #100
73     $display( "The number of success test cases:%d \n", counter );
74
75     /*-----Second Test Case-----*/
76
77     #20;
78
79     x = 4'b0000;
80     y = 4'b0001;
81
82     #50;
```

```

$display( "inputA:%d , inputB:%d , z:%d , v:%d n:%d \n",x , y , z , v , n ) ;

if ( z == 0 && n == 1 && v == 0 ) begin
    $display( "TestCase# 4 : SUCCESS \n" ) ;
    counter=counter+1;
end
else begin
    $display( "TestCase# 4 : FAILED \n" ) ;
end

#100
$display( "The number of success test cases:%d \n", counter ) ;

end


endmodule

```

```

# inputA:  5 , inputB:  3 , z: 0 , v: 0 n: 0
#
# TestCase# 1 : SUCCESS
#
# inputA: 5 , inputB: 5 , z:1 , v:0 n:0
#
# TestCase# 2 : SUCCESS
#
# The number of success test cases:                2
#
# inputA: 5 , inputB: 6 , z:0 , v:0 n:1
#
# TestCase# 3 : SUCCESS
#
# The number of success test cases:                3
#
# inputA: 0 , inputB: 1 , z:0 , v:0 n:1
#
# TestCase# 4 : SUCCESS
#
# The number of success test cases:                4
#

```

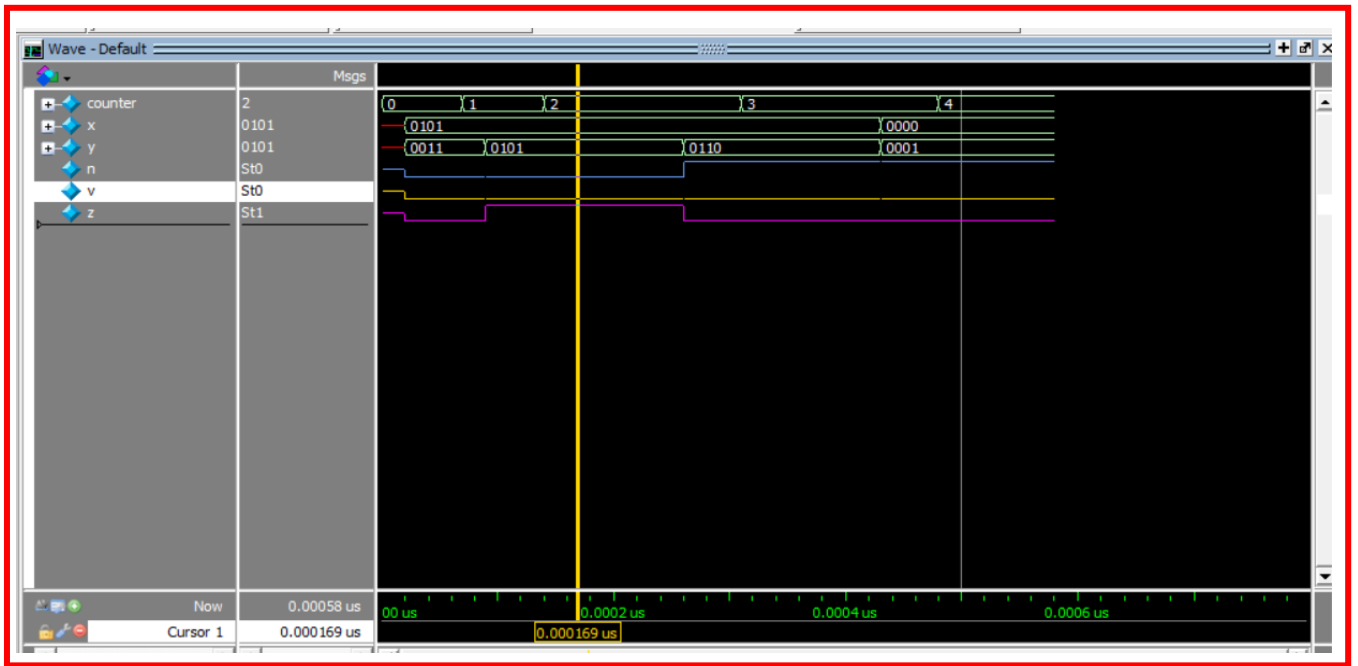

Comments

In the provided test bench and output waveform and displayed results we tried to verify the functionality of the four-bit comparator module by applying different test cases and checking the expected results. The implementation done following the given block diagram below. We verified the functionality of it by applying different test cases as the following:

$X = 0101$ and $Y = 0011$ □ The output is $N = 0$, $V = 0$, $Z = 0$

$X = 0101$ and $Y = 0101$ □ The output is $N = 0$, $V = 0$, $Z = 1$

$X = 0101$ and $Y = 0110$ □ The output is $N = 1$, $V = 0$, $Z = 0$

$X = 0000$ and $Y = 0001$ □ The output is $N = 1$, $V = 0$, $Z = 0$

➤ Bonus assignment

```
M E:/AUC assignments/Digital/lab4/Karim/BCD_ADDER.v - Default
Ln#
1 module BCD_adder_final( x , y , s2 , carry );
2
3     input [3:0] x;
4     input [3:0] y;
5     output reg [3:0] s2;
6     output reg carry;
7     reg [3:0] s;
8     always@(*) begin
9
10        {carry,s} = x+y;
11
12        if( carry || ( s[3] & s[2] ) || ( s[3] & s[1] ) ) begin
13            s2=s+4'b0110;
14        end
15
16        else begin
17            s2=s;
18        end
19    end
20 end
21 endmodule
22
```

Test bench

```
module test_bench_bcd();
    reg [3:0] x;
    reg [3:0] y;
    wire [3:0] s;
    wire carry;

    integer counter;

    BCD_adder_final BCD_adder_final1 ( x , y , s , carry );

    initial begin
        counter=0;

        /*-----First Test Case-----*/
        #20;

        x = 4'b0101;
        y = 4'b0101;

        #50;

        $display( "inputA:%d , inputB:%d , s:%d , carry:%d \n",x , y , s , carry ) ;

        if ( s == 4'b0000 && carry == 0 ) begin
            $display( "TestCase# 1 : SUCCESS \n" ) ;
            counter=counter+1;
        end
        else begin
            $display( "TestCase# 1 : FAILED \n" ) ;
        end

        /*-----Second Test Case-----*/
        #20;

        x = 4'b1001;
        y = 4'b1001;

        #50;

        $display( "inputA:%d , inputB:%d , s:%d , carry:%d \n",x , y , s , carry ) ;

        if ( s == 4'b1000 && carry == 1 ) begin
            $display( "TestCase# 2 : SUCCESS \n" ) ;
            counter=counter+1;
        end
    end
end
```

```

else begin
    $display( "TestCase# 2 : FAILED \n" );
end

/*-----Second Test Case-----*/

#20;

x = 4'b0111;
y = 4'b1000;

#50;

$display( "inputA:%d , inputB:%d , s:%d , carry:%d \n",x , y , s , carry );


if ( s == 4'b0101 && carry == 0 ) begin
    $display( "TestCase# 4 : SUCCESS \n" );
    counter=counter+1;
end
else begin
    $display( "TestCase# 4 : FAILED \n" );
end

#100
$display( "The number of success test cases:%d \n", counter );

end

endmodule

```

 

```
# inputA: 5 , inputB: 5 , s: 0 , carry:0
#
# TestCase# 1 : SUCCESS
#
# inputA: 9 , inputB: 9 , s: 8 , carry:1
#
# TestCase# 2 : SUCCESS
#
# inputA: 7 , inputB: 8 , s: 5 , carry:0
#
# TestCase# 4 : SUCCESS
#
# The number of success test cases:      3
#
```

Comments

In the above representation, The BCD_adder_final module is responsible for performing the addition of two BCD (Binary Coded Decimal) numbers. It takes two four-bit inputs (x and y) and produces a four-bit sum (s) and a carry output (carry). We make BCD Correction, after the addition of each digit, the module performs BCD correction if necessary. BCD correction ensures that the sum in each digit position remains a valid BCD digit (0-9). If the sum for a digit position exceeds 9, it means there is a carry to the next digit. In this case, the sum is adjusted by subtracting 10 or adding 6, and the carry output for that digit is set to 1. In the above test bench, when we add 9 and 9 the output will be 8 and the carry out will be 1 as the addition of them will be 18 and when we add 7 or subtract 10 the output will be 5 and the carry out will be 0 as the addition is less than 10 (not represented in 4 bits) and so on.