

# **Digital Design Lab 2**

## **Combinational Circuits**

**Name: Karim Mahmoud Kamal**

**AUC ID: V23010174**

**Section: 16**

**Eng. Mohamed El Shafey**

## 2x1 Multiplexer

### Structural Model:

```
module Mux2to1_gatelevel (I0, I1, select, Y);  
    input I0;  
    input I1;  
    input select;  
    output Y;  
    wire w1;  
    wire w2;  
    and g1(w1, I0, select);  
    and g2(w2, I1, ~select);  
    or g3(Y, w1, w2);  
endmodule
```

---

### Behavioral Model:

```
module mux2to1_behavioral (I0, I1, select, Y);  
    input I0;  
    input I1;  
    input select;  
    output reg Y;  
    always @ (*) begin
```

```
    if (select==0)
        Y=I0;
    else if (select==1)
        Y=I1;
    end
endmodule
```

---


**Dataflow Model:**

```
module mux2to1_data_flow (I0, I1, select, Y);
    input I0;
    input I1;
    input select;
    output Y;

    assign Y= (~select & I0) | (select & I1);
endmodule
```

---

### Netlist and symbol of the Mux:

 

### 4x1 Multiplexer

#### Structural Modeling:

```
module mux4to1_structural (I, S, Y);
```

```
    input [3:0] I;
```

```
    input [1:0] S;
```

```
    output Y;
```

```
    wire w1;
```

```
    wire w2;
```

```
    wire w3;
```

```
    wire w4;
```

```
    and g1(w1, ~S[1], ~S[0], I[0]);
```

```
    and g2(w2, ~S[1], S[0], I[1]);
```

```
    and g3(w3, S[1], ~S[0], I[2]);
```

```
and g4(w4, S[1], S[0], I[3]);
```

```
or g5(Y, w1, w2, w3, w4);
```

```
endmodule
```

---

### behavioral Modeling:

```
module mux4to1_behavioral (I, S, Y);
```

```
    input [3:0] I;
```

```
    input [1:0] S;
```

```
    output reg Y;
```

```
    always @ (I or S)
```

```
    begin
```

```
        case (S)
```

```
            2`b00 : Y=I[0];
```

```
            2`b01 : Y=I[1];
```

```
            2`b10 : Y=I[2];
```

```
            2`b11 : Y=I[3];
```

```
        endcase
```

```
    end
```

endmodule


---

### DataFlow Modeling:

```
module mux4to1_dataflow (I, S, Y);  
  
    input [3:0] I;  
  
    input [1:0] S;  
  
    output Y;  
  
    assign Y=(~S[1] & ~S[0] & I[0]) |  
            (~S[1] & S[0] & I[1]) | (S[1] & ~S[0] &  
            I[2]) | (S[1] & S[0] & I[3]);  
  
endmodule
```

---

### Netlist

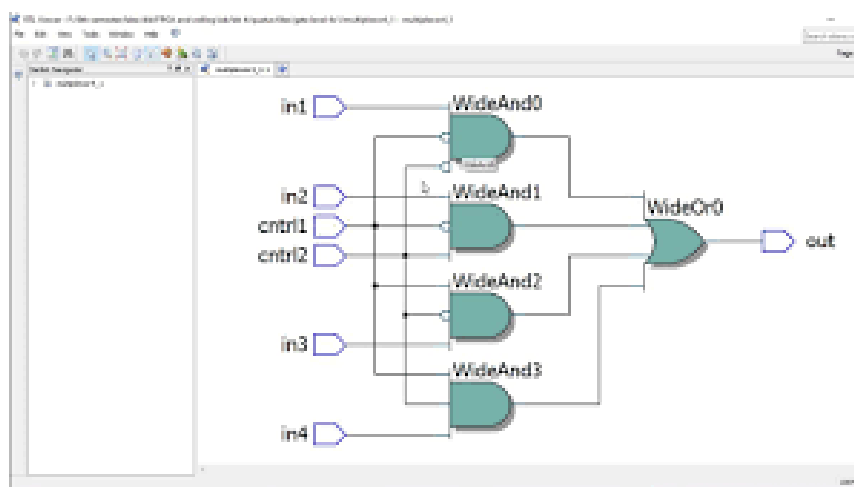

## Decoder

### DataFlow Modeling:

```
module decoder_data_flow (A, B, C, D);  
    input A;  
    input B;  
    input C;  
    output [7:0]D;  
    assign D[0]=~A & ~B & ~C;  
    assign D[1]=~A & ~B & C;  
    assign D[2]=~A & B & ~C;  
    assign D[3]=~A & B & C;  
    assign D[4]=A & ~B & ~C;  
    assign D[5]=A & ~B & C;  
    assign D[6]=A & B & ~C;  
    assign D[7]=A & B & C;  
endmodule
```

---

### behavioral Modeling:

```
module decoder_behavioral (I, D);  
    input [2:0] I;  
    output reg [7:0] D;
```

```

always @ (I)
begin
    case (I)
        3`b000: D=8`b10000000;
        3`b001: D=8`b01000000;
        3`b010: D=8`b00100000;
        3`b011: D=8`b00010000;
        3`b100: D=8`b00001000;
        3`b101: D=8`b00000100;
        3`b110: D=8`b00000010;
        3`b111: D=8`b00000001;
    endcase
end
endmodule

```

---

### Display Adder

#### Model for Adder Module:

```

module adderx (a, b, s, c);
    input a, b;
    output s, c;

```



```
    assign s = a ^ b; // sum using xor  
    assign c = a & b; // carry  
endmodule
```

---

**Model for Decoder Module:**

```
module decoderx (s0, s1, a, b, c, d, e, f, g);  
input s0, s1;  
output a, b, c, d, e, f, g;  
  
    assign a = ~s0;  
    assign b = 1;  
    assign c = ~s1;  
    assign d = ~s0;  
    assign e = ~s0;  
    assign f = ~s1 & ~s0;  
    assign g = s1 & ~s0;  
endmodule
```

---

### Model for Top Module:

```
module Display_adder (x, y, a, b, c, d, e, f, g);  
    input x, y;  
    output a, b, c, d, e, f, g;  
    wire w0, w1;  
    adderx U1 (x, y, w0, w1);  
    decoderx U2 (w0, w1, a, b, c, d, e, f, g);  
endmodule
```

---

### Comparator

#### Behavioral Modeling:

```
module magcomp (A,B,Gt,Lt,Eq);  
    input [7:0]A,B;  
    output  Gt,Lt,Eq;  
    reg  Gt, Lt, Eq;  
    always @ (A or B)  
  
    begin  
        Gt <= ( A > B )? 1'b1 : 1'b0;  
        Lt <= ( A < B )? 1'b1 : 1'b0;  
        Eq <= ( A == B )? 1'b1 : 1'b0;
```

```
end  
endmodule
```

---

### **Lab 3 Assignment**

#### **Half Adder Module:**

```
module half_adder ( a , b , sum , carry );  
    input a,b;  
    output sum, carry;  
  
    xor x1 ( sum, a , b );  
    and a1 ( carry , a , b );  
endmodule
```

---

#### **Full Adder Module:**

```
module full_adder ( in1 , in2 , Cin , sum , carry );  
    input in1, in2, Cin;  
    output sum, carry;  
    wire ws1, wc1, wc2;
```

```
half_adder ha1 ( in1 , in2 , ws1 , wc1 );  
  
half_adder ha2 ( ws1 , Cin , sum , wc2 );  
  
or r1 ( carry , wc1 , wc2 );  
  
endmodule
```

---

#### **Four Bit Comparator Module:**

```
module four_bit_comparator( x , y , v , n , z );  
  
    input [3:0] x;  
  
    input [3:0] y;  
  
    output v,n,z;  
  
    wire s0,s1,s2,s3;  
  
    wire c1,c2,c3,c4;  
  
    full_adder fa1 ( x[0] , ~y[0] , 1'b1 , s0 , c1 );  
  
    full_adder fa2 ( x[1] , ~y[1] , c1 , s1 , c2 );  
  
    full_adder fa3 ( x[2] , ~y[2] , c2 , s2 , c3 );  
  
    full_adder fa4 ( x[3] , ~y[3] , c3 , s3 , c4 );  
  
    nor nor1 ( z , s0 , s1 , s2 , s3 );  
  
    xor xor1 ( v , c3 , c4 );  
  
    assign n = s3;  
  
endmodule
```

---

## **Bonus**

### **BCD Adder Module**

```
module BCD_adder( x , y , s , carry );  
  
    input [3:0] x;  
  
    input [3:0] y;  
  
    output [3:0] s;  
  
    output carry;  
  
    wire s0, s1, s2, s3;  
  
    wire c1, c2, c3, c4;  
  
    full_adder fa1 ( x[0] , y[0] , 1'b0 , s0 , c1 );  
  
    full_adder fa2 ( x[1] , y[1] , c1 , s1 , c2 );  
  
    full_adder fa3 ( x[2] , y[2] , c2 , s2 , c3 );  
  
    full_adder fa4 ( x[3] , y[3] , c3 , s3 , c4 );  
  
    assign carry = c4;  
  
endmodule
```

### **8-Bit BCD Adder**

```
module BCD_adder_final( x , y , s , carry, carry2 );  
  
    input [3:0] x;  
  
    input [3:0] y;  
  
    output [3:0] s;
```

```

output carry , carry2;

wire [3:0] ss;

wire c1, w1 ,w2;

BCD_adder bcd1 ( x , y , ss , c1 );

and a1 ( w1 , ss[3] , ss[2] );

and a2 ( w2 , ss[3] , ss[1] );

or o1 ( carry , w1 , w2 , c1 );

BCD_adder bcd2 ( ss , {1'b0,carry,carry,1'b0}, s , carry2 );

endmodule

```

```

//----- behavioral -----

```

```

module behavioral_four_bit_comparator( x , y , v , n , z );

```

```

    input [3:0] x;

```

```

    input [3:0] y;

```

```

    output v,n,z;

```

```

    reg v,n,z;

```

```

    always @ (*) begin

```

```

        case({x,y})

```

```

            8'b0000_0000: begin

```

```

                v= 1'b0;

```

```

                z= 1'b1;

```

```

                n= 1'b0;

```

**end**

**8'b1111\_1111: begin**

**v= 1'b0;**

**z= 1'b1;**

**n= 1'b0;**

**end**

**8'b1000\_0000: begin**

**v= 1'b0;**

**z= 1'b0;**

**n= 1'b1;**

**end**

**8'b0000\_1000: begin**

**v= 1'b0;**

**z= 1'b1;**

**n= 1'b0;**

**end**

**8'b0001\_0000: begin**

**v= 1'b1;**

**z= 1'b0;**

**n= 1'b1;**

**end**

**8'b0000\_0001: begin**

**v= 1'b0;**

**z= 1'b0;**

**n= 1'b0;**

**end**

**8'b1011\_1001: begin**

**v= 1'b0;**

**z= 1'b0;**

**n= 1'b1;**

**end**

**8'b1100\_1001: begin**

**v= 1'b0;**

**z= 1'b0;**

**n= 1'b0;**

**end**

**8'b1010\_0010: begin**

**v= 1'b0;**

**z= 1'b0;**

**n= 1'b0;**

**end**

**8'b0101\_1100: begin**

**v= 1'b;**



```

        z= 1'b;

        n= 1'b;

    end

endcase

end

endmodule

```

---

### Behavioral of BCD Adder

```

module modulebcdadd (cin, X, Y, S, cout);

input cin;

input [3:0] X, Y;

output reg [3:0] S;

output reg cout;

reg [4:0] Z;

always @(X, Y, cin)

    begin

        Z = X + Y + cin;

        if (Z < 10)

            {cout, S} = Z;

        else


            {cout, S} = Z + 6;

```


---

end  
endmodule


## 8-Bit BCD Adder Netlist

 


## Test Bench of Full Adder

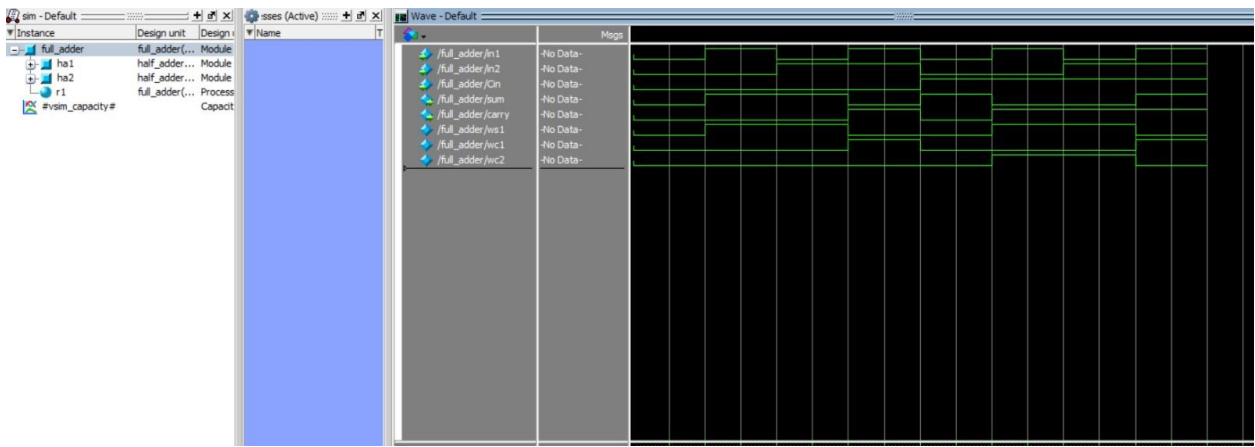


## Test Bench of Half Adder

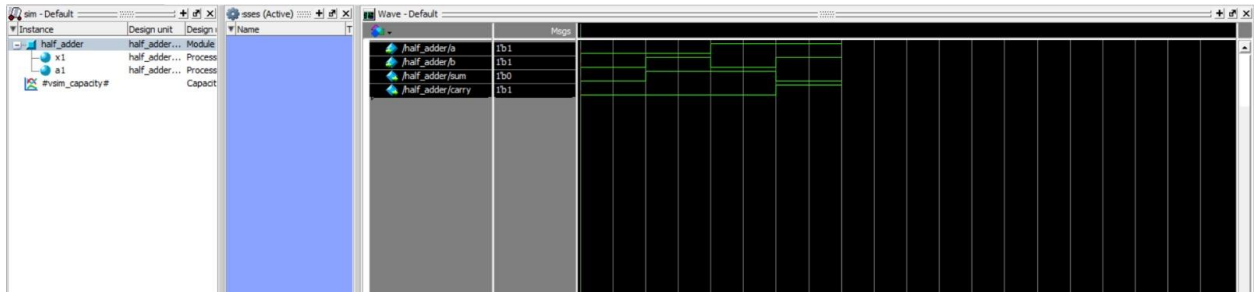


## Test Bench of 4-bit Comparator

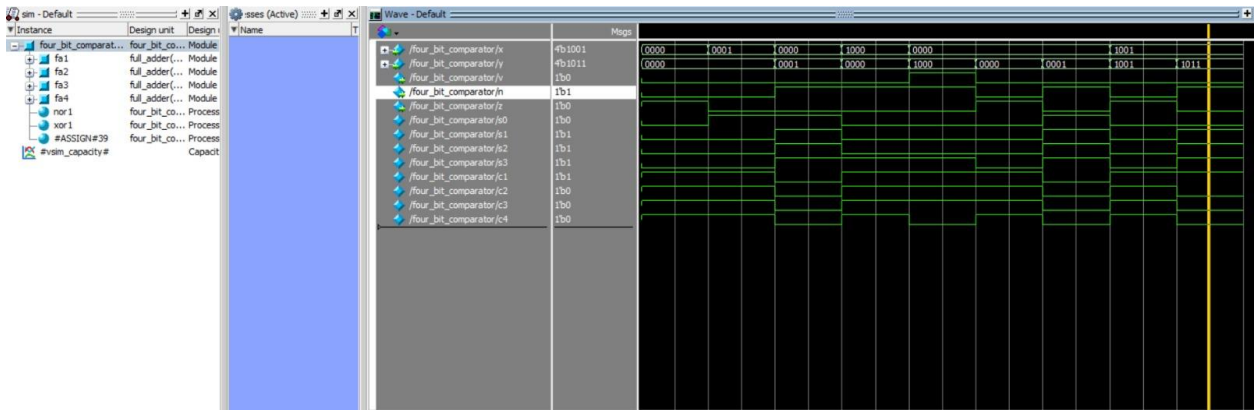


## Netlist of 4-Bit BCD Adder

 

### Netlist of Full Adder

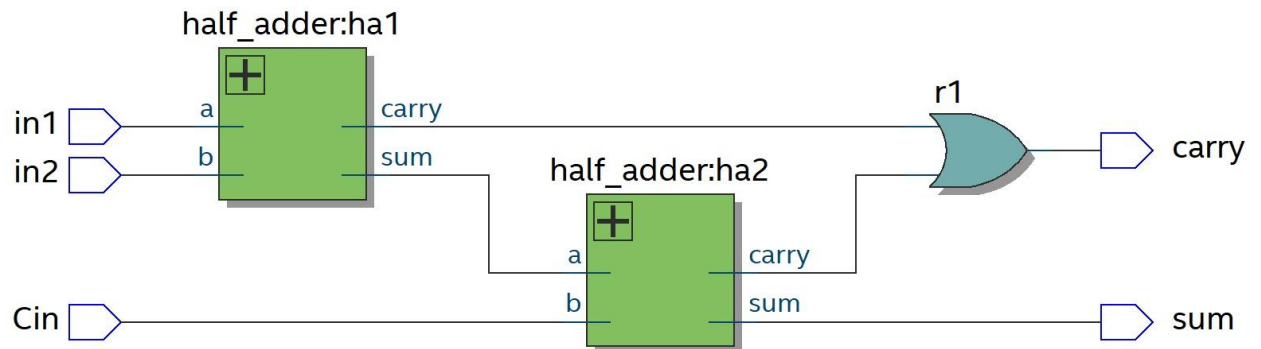

### Netlist of Half Adder

 

## Netlist of Comparator

