






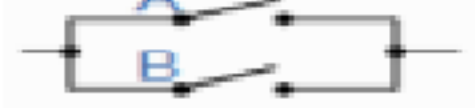



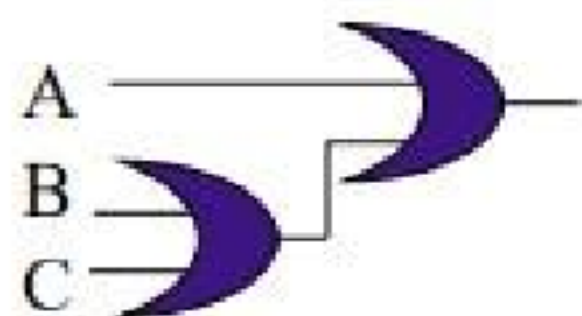
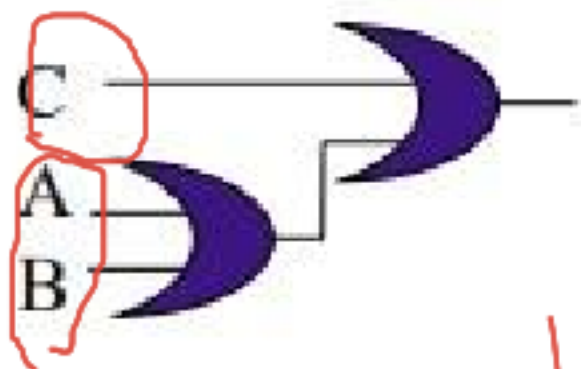
Boolean Algebra Laws

Associative laws	$(a \cdot b) \cdot c = a \cdot (b \cdot c)$	$(a + b) + c = a + (b + c)$
Commutative laws	$a \cdot b = b \cdot a$	$a + b = b + a$
Distributive laws	$a \cdot (b + c) = a \cdot b + a \cdot c$	$a + (b \cdot c) = (a + b) \cdot (a + c)$
Identity laws	$a \cdot 1 = a$	$a + 0 = a$
Compliment laws	$a \cdot a' = 0$	$a + a' = 1$
Double Negation Law	$\underline{\underline{A'' = A}}$	



Boolean Expression	Equivalent Switching Circuit
$A + 1 = 1$	
$A + 0 = A$	
$A \cdot 1 = A$	
$A \cdot 0 = 0$	
$A + A = A$	
$A \cdot A = A$	
$A + \bar{A} = 1$	
$A \cdot \bar{A} = 0$	
$A + B = B + A$	
$A \cdot B = B \cdot A$	

Why ?

Timing!



$$(A+B)+C \quad / \quad (A+B)C + A$$

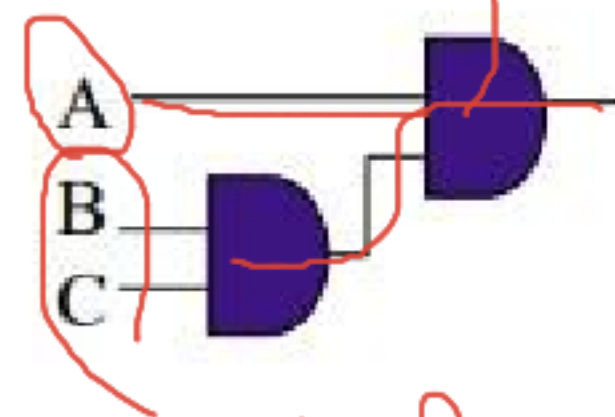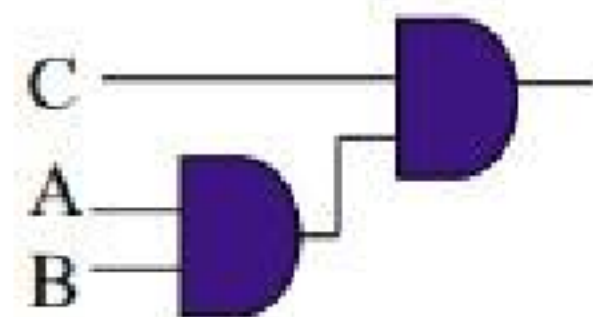

$$(A.B).C \quad / \quad (B.C).A$$

Why Simplifying Boolean Algebra?

- Gate-level minimization

- Absorptive Law: This law enables a reduction in a complicated expression to a simpler one by absorbing like terms.

~~$A + (A \cdot B) = A$~~
1- $A + (A \cdot B) \rightarrow A \cdot 1 + (A \cdot B) \Rightarrow A \cdot (1 + B) + A \cdot B$

2- $A(A + B) \rightarrow A + AB = A$

3- $A + A'B$

$A \cdot 1 + \bar{A}B = A(1 + B) + \bar{A}B$

$A + AB + \bar{A}B = A + \cancel{A}B + \bar{A}B = A + (A + \bar{A})B$
 $= \boxed{A + B}$ ✓

$A + AB + \cancel{A}B = A + AB$
 $A(1 + B) = A$

Prove that: $A + A'B$ $= A + B$ ✓

- Simplify the following Boolean expression:

- $F(A, B, C, D) = \underline{A'BCD} + \underline{AB'CD'} + \underline{AB'CD} + \underline{ABC'D} + \underline{ABCD'} + \underline{ABCD}$

ABD

$$\bar{A}BCD + ABCD = (\bar{A} + A)BCD = BCD$$

$$A\bar{B}\bar{C}\bar{D} + A\bar{B}CD + A\bar{B}C\bar{D} + A\bar{B}CD$$

$$A\bar{C}\bar{D}$$

$$ACD$$

$$AC$$


$$AC + BCD + A\bar{B}D = A(C + BD)(C + A)$$

DeMorgan's Theorem

- The complement of the product is the sum of the complements.
- The complement of the sum is the product of the complements.

$$\overline{A+B} \equiv \bar{A} \cdot \bar{B} \rightarrow \text{Truth table}$$
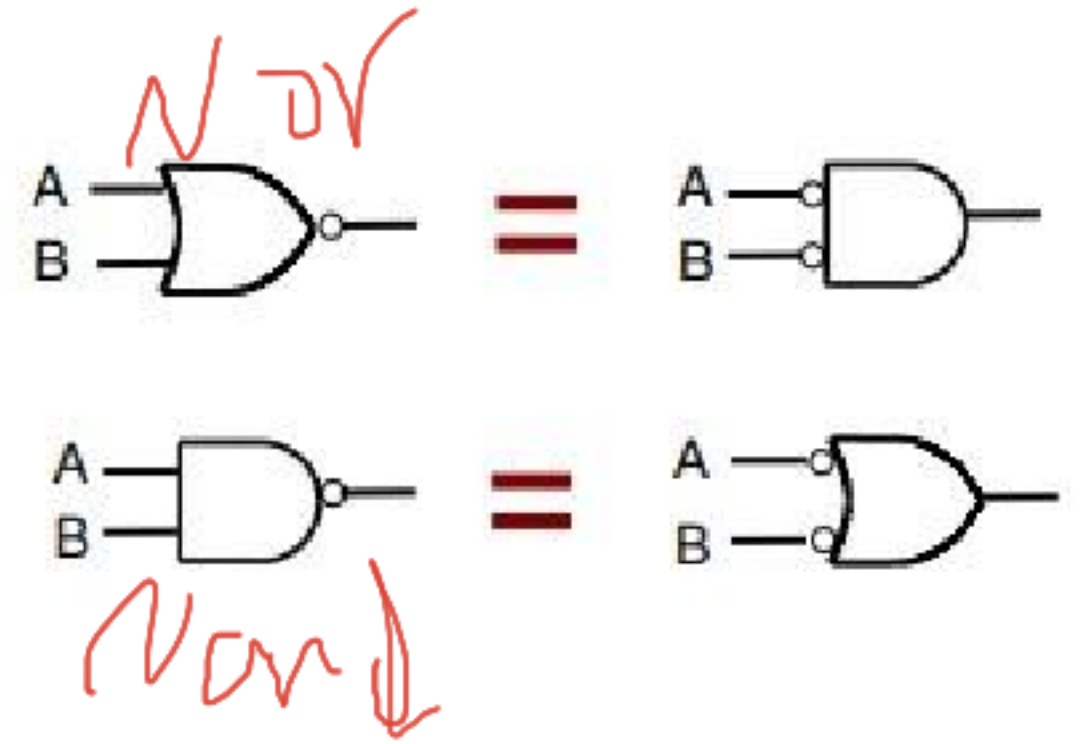
$$\overline{A \cdot B} \equiv \bar{A} + \bar{B} \rightarrow \text{" "}$$



$$Y = \overline{(A + BD)C} = (A + \overline{BD}) + \overline{C}$$

$$= (\overline{A} \cdot \overline{BD}) + C$$

$$= (\overline{A} \cdot B \cdot D) + C$$


$$Y = \overline{(\overline{ACE + D})} + B = (\overline{ACE + D}) \cdot \overline{B}$$

$$= (\overline{ACE} \cdot \overline{D}) \cdot \overline{B}$$

$$= ((\overline{A} + \overline{C} + \overline{E}) \cdot D) \cdot \overline{B}$$

$$\boxed{(\overline{A} + \overline{C} + \overline{E}) \cdot D \cdot \overline{B}}$$

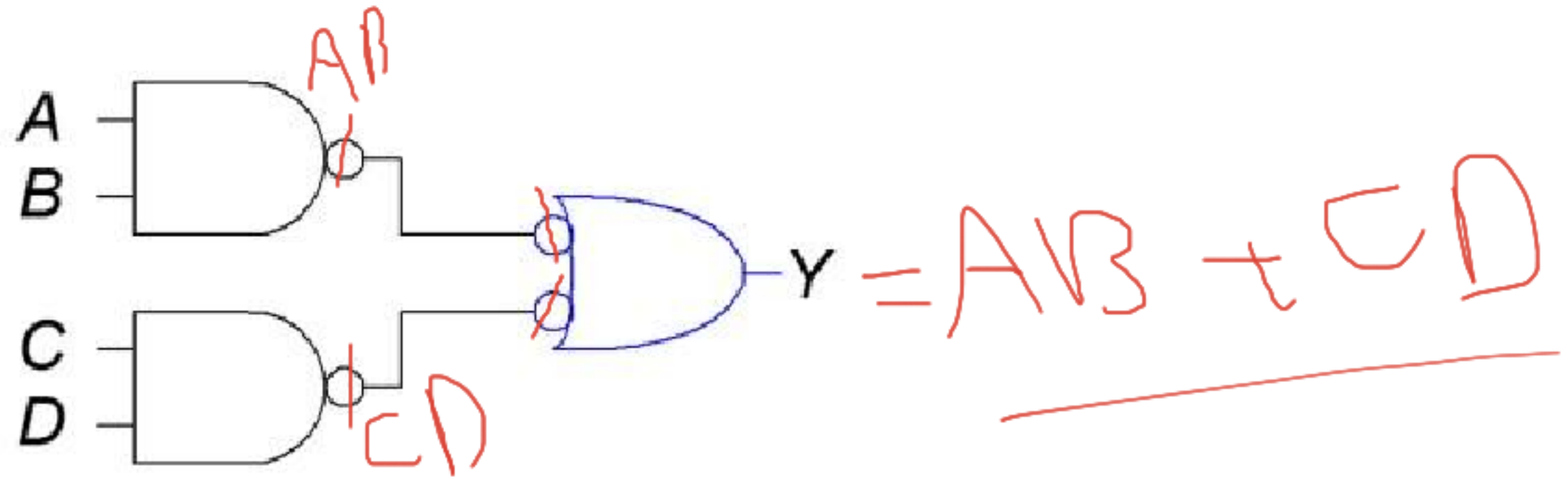- What is the Boolean expression for this circuit?



Consensus Theorem

$$AB + A'C + BC = AB + A'C \implies \text{ANDing form}$$

Proof:

$$AB + \bar{A}C + BC \cdot 1$$

$$AB + \bar{A}C + ABC + \bar{A}BC$$

$$AB +$$

$$\bar{A}C$$

Verify Using Truth Table
 \implies They must be the same

$$\bar{A}C \cdot B$$

$$(A+B)(A'+C)(B+C) = (A+B)(A'+C) \Rightarrow \text{ORing form}$$

$$(AB+AC+\cancel{B}+\cancel{BC})(A+C)$$

$$(\cancel{B}+AB+AC)(\bar{A}+C)$$

$$(B+AC)(\bar{A}+C)$$

$$B(\bar{A}+C) + \cancel{AC(\bar{A}+C)} \quad AC + A\bar{A}$$

$$B(\bar{A}+C) + A(\bar{A}+C)$$

$$(\bar{A}+C)(A+B)$$

$$\cancel{A\bar{A}} + AC$$

K-map:

a graphical representation used in digital design and logic optimization to simplify Boolean algebra expressions and reduce the number of logic gates required.

K-maps are particularly useful for minimizing logic functions.


Gray code ensures that only one variable/bit changes between each pair of adjacent cells.



Rules:

- Every 1 must be circled at least once ✓
- Each circle must span a power of 2 (i.e. 1, 2, 4) squares in each direction ✓
- Each circle must be as large as possible ✓
- A circle may wrap around the edges
- A “don't care” (X) is circled only if it helps minimize the equation

1,2,3,4

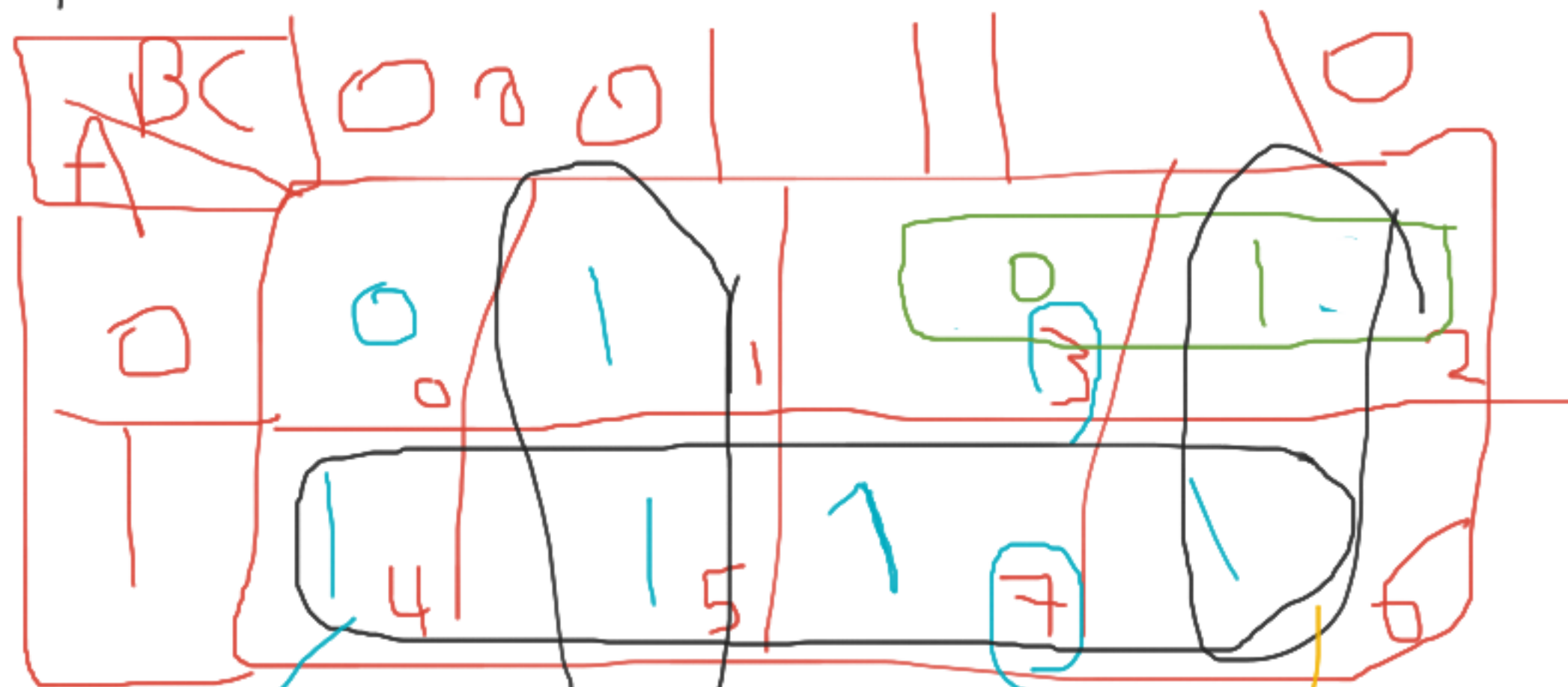

	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

$$A + \overline{B}C + B\overline{C}$$

$$A + (B \oplus C)$$

Notes

1	1	1	
1	1	1	
	1	1	
1	1	1	

1	1	1	
1	1	1	
	1	1	
1	1	1	

1			
1			
1			1
1	1	1	

1	1		1
		1	
1	1		


A \ B	0	1
0	0	1
1	1	0

WRONG X

0

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

15

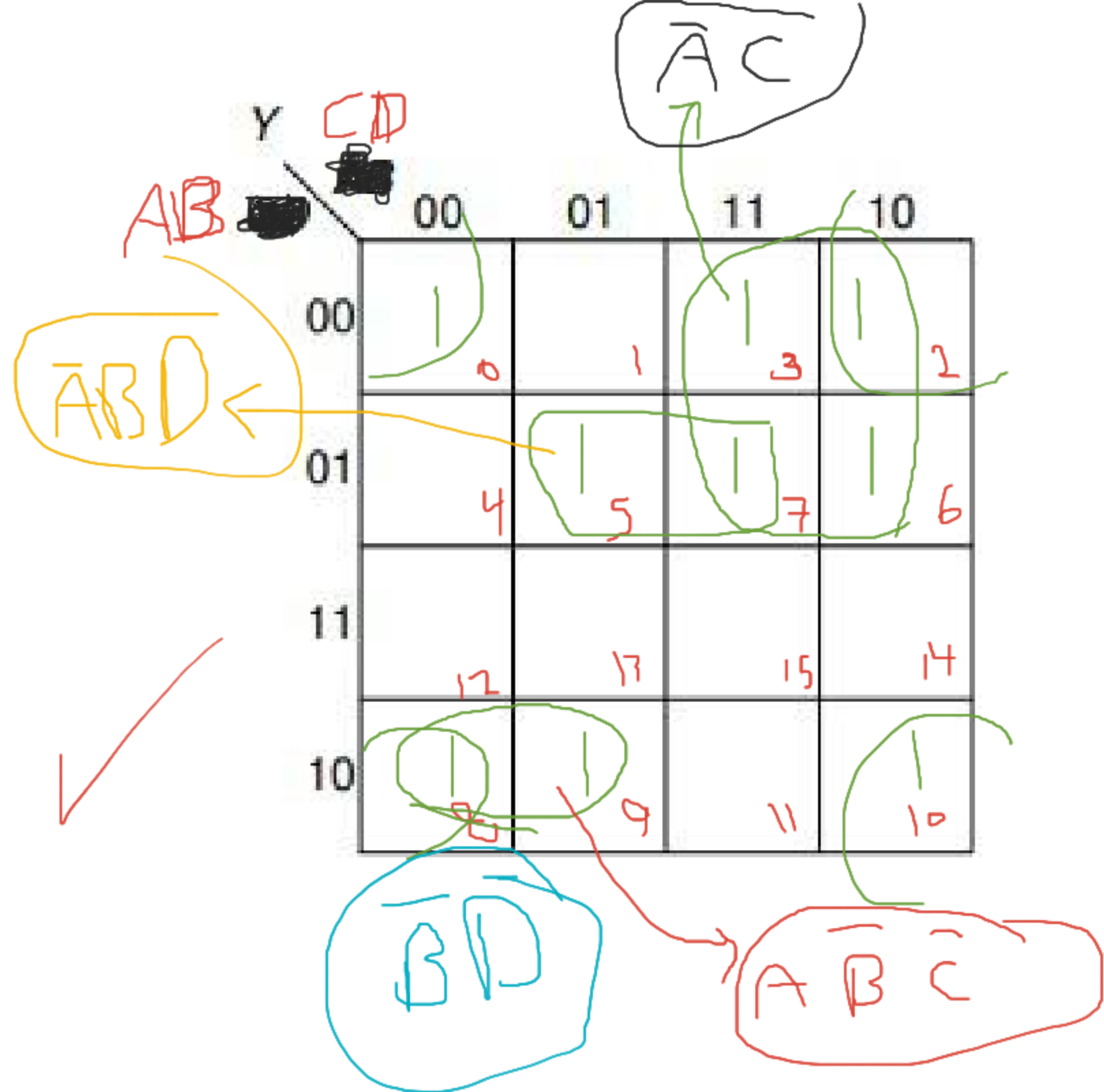

- don't cares can be treated as 1s or 0s
- depending on which is more advantageous

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

$A + C + \overline{B}\overline{D}$

AB

A

$\overline{B}\overline{D}$

